

main (1 of 1)

Draw a truth table for each circuit. What is the boolean operation?

